

Boolean algebra

Objectives:

- 1- Basic rules of Boolean algebra.
- 2- De Morgan's theorems.
- 3- Boolean expression for a logic circuit.
- 4- The sum of product (SOP) form.
- 5- The product of sum (POS) form.
- 6- Examples

1-Basic rules of Boolean algebra

1.1- Boolean Addition (OR gate)

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A = A$$

$$A + \bar{A} = 1$$

1.2- Boolean Multiplication (AND gate)

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A \cdot A = A$$

$$A \cdot \bar{A} = 0$$

1.3-Commutative laws

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

1.4- Associative laws

$$A + (B + C) = (A + B) + C$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

1.5-Distribution law

$$A \cdot (B + C) = AB + AC \quad (\text{Left distribution law})$$

$$(B + C) \cdot A = BA + CA \quad (\text{Right distribution law})$$

1.6- Double complement theorem

$$\overline{\overline{A}} = A \qquad \overline{\overline{\overline{A}}} = \overline{A}$$

2- De Morgan's theorem

$$\overline{(A + B)} = \overline{A} \cdot \overline{B}$$

$$\overline{(A \cdot B)} = \overline{A} + \overline{B}$$

Other theorem can be derived from the basic laws above:

$$1- A+AB=A$$

$$2- AB+A\bar{B}=A$$

$$3- (A+\bar{B}).B=AB$$


$$4- (A+A).(A+\bar{B})=A$$

$$5- (A+B).(A+C)=A+BC$$

$$6- A(A+B)=A$$

$$7- A+\bar{A}B=A+B$$

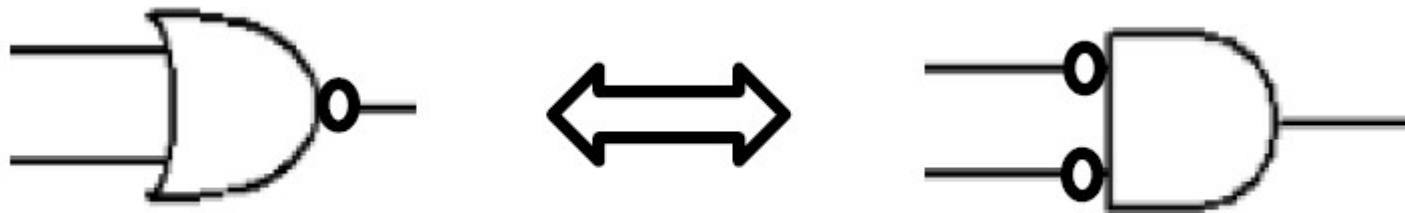Example-1: prove $\overline{A+B} = \bar{A} \cdot \bar{B}$



X	Y	\bar{A}	\bar{B}	$\overline{(A + B)}$	$\bar{A}.\bar{B}$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

Example-2: Apply De Morgan's theorem to the expressions \overline{XYZ} and $\overline{X + Y + Z}$

Solution:

$$1) \quad \overline{XYZ} = \overline{X} + \overline{Y} + \overline{Z}$$

$$2) \quad \overline{X + Y + Z} = \overline{X} \overline{Y} \overline{Z}$$

Home work: Apply De Morgan theorems to each of the following expressions.

$$1) \overline{(A + B + C)D}$$

$$2) \overline{ABC + DEF}$$

$$3) \overline{\overline{(A + B)} + \overline{\overline{C}}}$$

Home work: Apply De Morgan's theorems to each of the following expressions.

(a) $\overline{(\overline{A + B}) + \overline{C}}$

(b) $\overline{(\overline{A} + B) + CD}$


(c) $\overline{(A + B)\overline{C}\overline{D} + E + \overline{F}}$

3- Boolean expression for logic circuit:

Example-3:


For the example circuit in Figure below, the Boolean expression is determined in the following three steps:

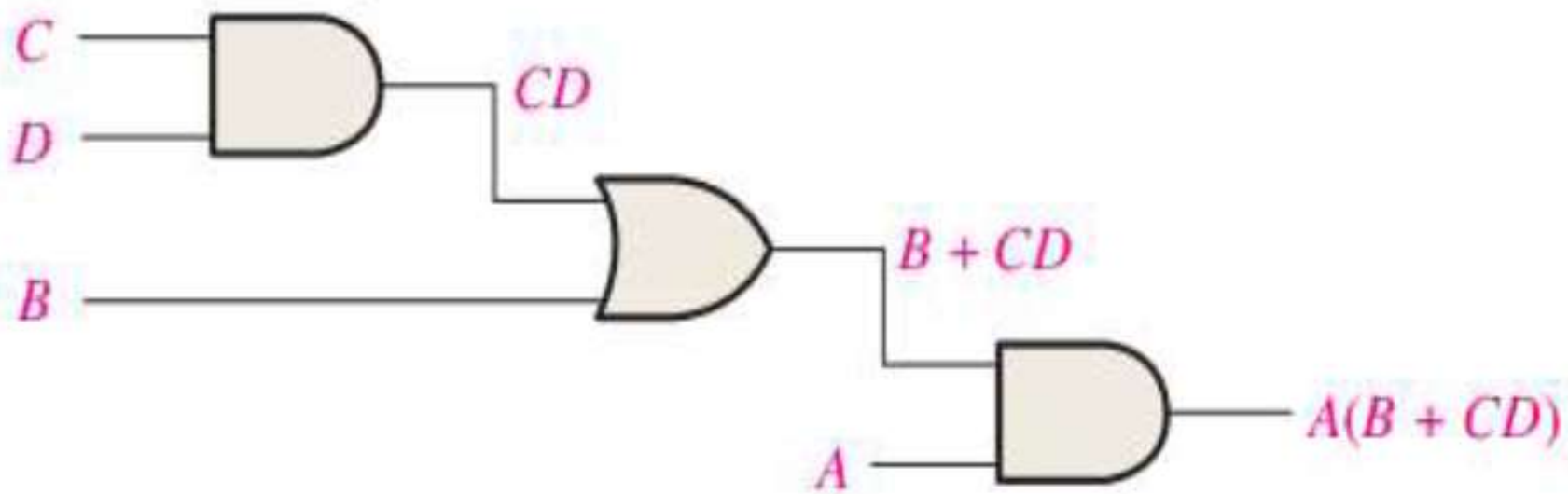1. The expression for the left-most AND gate with inputs C and D is CD .
2. The output of the left-most AND gate is one of the inputs to the OR gate and B is the other input. Therefore, the expression for the OR gate is $B + CD$.
3. The output of the OR gate is one of the inputs to the right-most AND gate and A is the other input. Therefore, the expression for this AND gate is $A(B + CD)$, which is the final output expression for the entire circuit.



Example-4: Using Boolean algebra techniques, simplify this expression and draw the logic circuit

$$F = (AB + A(B + C) + B(B + C))$$

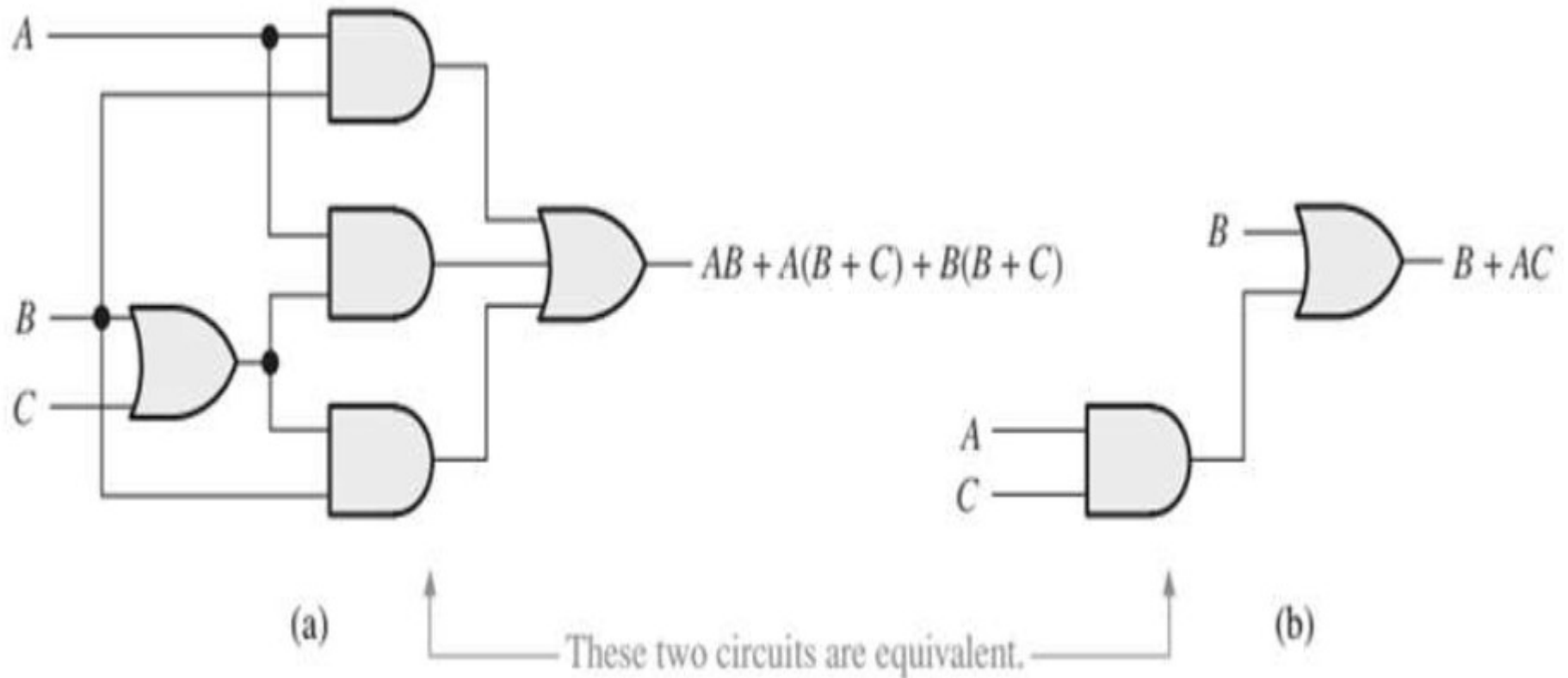

Solution:

$$\begin{aligned} & AB + A(B + C) + B(B + C) \\ &= AB + AB + AC + BB + BC \\ &= (AB + AB) + AC + (B + BC) \\ &= AB + AC + B \\ &= B + AC \end{aligned}$$

Example-5: Simplify the following Boolean
expression: $AB + AC + \bar{A} \bar{B} C$

Solution:

$$\begin{aligned} & \overline{(AB)} \overline{(AC)} + \bar{A} \bar{B} C \\ = & (\bar{A} + \bar{B})(\bar{A} + \bar{C}) + \bar{A} \bar{B} C \\ = & \bar{A} \bar{A} + \bar{A} \bar{C} + \bar{A} \bar{B} + \bar{B} \bar{C} + \bar{A} \bar{B} C \\ = & \bar{A} + \bar{A} \bar{C} + \bar{A} \bar{B} + \bar{B} \bar{C} \\ = & \bar{A} + \bar{B} \bar{C} \end{aligned}$$

Home work: Draw the logic diagrams for the following Boolean expressions

$$1) \quad Y = \bar{A}\bar{B} + B(A + C)$$

$$2) \quad Y = BC + A\bar{C}$$

$$3) \quad Y = A + CD$$

$$4) \quad Y = (A + B)(\bar{C} + D)$$

4-The sum Of products (SOP) Form

A product term was defined as term consisting of product of variable or their complements.

When two or more product terms are summed by Boolean addition, the resulting expression is a sum of product (SOP). Some example are:

$$AB + ABC$$

$$ABC + CDE + \bar{B}C\bar{D}$$

$$\bar{A}B + \bar{A}B\bar{C} + AC$$

5-The product of sums (POS) Form

A sum term was defined as term consisting of sum of variables or their complements. When two or more sum terms are multiplied, the resulting expression is a product of sums (POS).

Some example are:

$$(\bar{A} + B)(A + \bar{B} + C)$$

$$(\bar{A} + \bar{B} + \bar{C})(C + \bar{D} + E)(\bar{B} + C + D)$$

$$(A + B)(A + \bar{B} + C)(\bar{A} + C)$$

Consider the truth table (T.T) for three variables given below using SOP and POS

X	Y	Z	SOP (Minterms)	Designation	POS (Maxterms)	Designation
0	0	0	$\bar{X}\bar{Y}\bar{Z}$	m0	$X + Y + Z$	M0
0	0	1	$\bar{X}\bar{Y}Z$	m1	$X + Y + \bar{Z}$	M1
0	1	0	$\bar{X}Y\bar{Z}$	m2	$X + \bar{Y} + Z$	M2
0	1	1	$\bar{X}YZ$	m3	$X + \bar{Y} + \bar{Z}$	M3
1	0	0	$X\bar{Y}\bar{Z}$	m4	$\bar{X} + Y + Z$	M4
1	0	1	$X\bar{Y}Z$	m5	$\bar{X} + Y + \bar{Z}$	M5
1	1	0	$XY\bar{Z}$	m6	$\bar{X} + \bar{Y} + Z$	M6
1	1	1	XYZ	m7	$\bar{X} + \bar{Y} + \bar{Z}$	M7

Example-6: Drive Boolean expression (B.E) using SOP and POS methods for 3-inputs & the output will be high (1) when the binary input values equal (1,4,7).

Solution:

$$\text{In SOP; } F = \sum m(1,4,7) = m_1 + m_4 + m_7 = \bar{X}\bar{Y}Z + X\bar{Y}\bar{Z} + XYZ$$

$$\text{In POS; } F = \pi M(0,2,3,5,6)$$

$$= (X + Y + Z) \cdot (X + \bar{Y} + Z) \cdot (X + \bar{Y} + \bar{Z}) \cdot (\bar{X} + Y + \bar{Z}) \cdot (\bar{X} + \bar{Y} + Z)$$

Example-7: From the truth table below, determine the standard SOP expression and the equivalent standard POS expression.

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1

Solution: There are four 1s in the output:

$$011 = \bar{X}YZ$$

$$100 = X\bar{Y}\bar{Z}$$

$$110 = XY\bar{Z}$$

$$111 = XYZ$$

$$F = \bar{X}YZ + X\bar{Y}\bar{Z} + XY\bar{Z} + XYZ$$

(For the SOP expression, the output is 1)

For the POS expression, the output is 0:

$$000 = X + Y + Z$$

$$001 = X + Y + \bar{Z}$$

$$010 = X + \bar{Y} + Z$$

$$101 = \bar{X} + Y + \bar{Z}$$

The resulting standard POS expression for the output F is

$$F = (X + Y + Z)(X + Y + \bar{Z})(X + \bar{Y} + Z)(\bar{X} + Y + \bar{Z})$$

Example-8: Design a logic circuit with 3-inputs and the output will be high (1) when the binary input values less than 3 using SOP & POS methods.

Solution:

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$\text{SOP: } F = \bar{X}\bar{Y}\bar{Z} + \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z}$$

$$\text{POS: } F = (X + \bar{Y} + \bar{Z})(\bar{X} + Y + Z)(\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + Z)(\bar{X} + \bar{Y} + \bar{Z})$$

Example- 9: Design a logic circuit with 3-inputs & the output will be high (1) when a majority of inputs are high (1) using SOP & POS methods;

Solution:

$$\text{SOP: } F = \bar{X}YZ + X\bar{Y}Z + XY\bar{Z} + XYZ$$

$$\text{POS: } F = (X + Y + Z)(X + Y + \bar{Z})(X + \bar{Y} + Z)(\bar{X} + Y + \bar{Z})$$

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

1) References

- 1) Digital Fundamentals, Thomas L. Floyd, Eleventh Edition, 2015, Pearson.
- 2) Digital design, M. Morris Mano and Michael D. Ciletti, Fifth Edition, 2013, Pearson.

Thank you
With best wishes