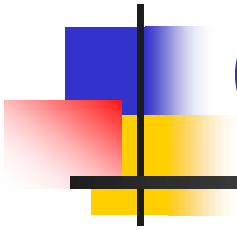


Unit 2 Part I

Combinational Circuits





HALF-ADDER

+

x

y

C

S


- **Half-adder:** Performs the most basic digital arithmetic operation, that is, **the addition of two binary numbers**.
- The half-adder requires two outputs because the sum $1 + 1$ is binary 10. The two inputs are:
called S (for sum) and C (for carry out).

From the truth table write the Boolean function outputs for the sum S and the carry out C:

$$S = x'y + xy' \text{ (Exclusive OR)}$$

$$C = xy \text{ (AND)}$$


(Logic diagram)

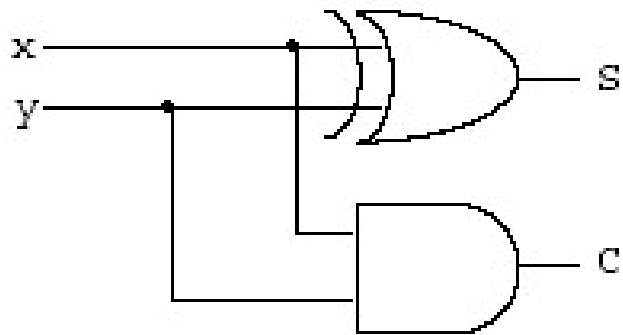

(Truth table for half-adder)

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

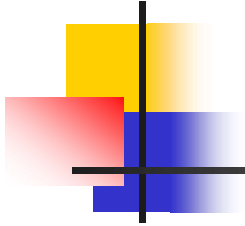Here is a proof of the Exclusive OR identity using truth table.




(Proof by truth table)

x	y	$x' y$	$x y'$	$x' y + x y'$
0	0	0	0	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

FULL-ADDER

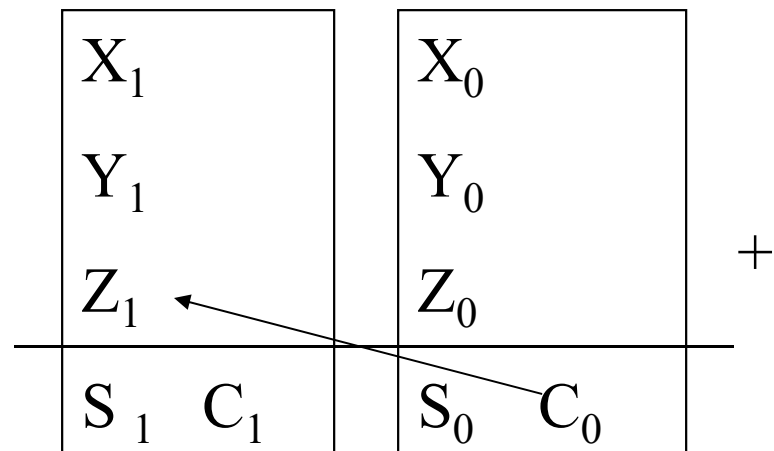- To implement an arithmetic adder for multiple-bit inputs, we need to treat the **carry out from the lower bit as a third input** (it becomes carry in for the current bit) in addition to the two input bits at the current bit position.



Full- Adder

It adds 3-bits, it has 3-inputs and 2-outputs



We will use x, y and z for inputs and s for sum and c for carry are the two outputs.

The truth table

x	y	z	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



Full Adder

$$S = x'y'z + x'yz' + xy'z' + xyz$$

k-map for s

$\begin{array}{c} yz \\ \diagdown \\ x \end{array}$	00	01	11	10
0	0	1	0	1
1	1	0	1	0



Full Adder

Inputs			Outputs	
x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = x \oplus y \oplus z$$



K-map on C

$$C = yz + xz + xy$$

But we would like to use the previous logic gate XOR

$\begin{array}{c} yz \\ x \end{array}$	00	01	11	10
0	0	0	1	0
1	0	1	1	1


The Karnaugh map shows three groups of 1s circled: a vertical orange oval around the 1 in row 0, column 11; a horizontal cyan oval around the 1s in row 1, columns 01 and 11; and a horizontal yellow oval around the 1s in row 1, columns 11 and 10.



K-map on C

We can write $C = x'y z + x y' z + x y z + x y z'$
 $= z(x'y + xy') + xy(z+z')$
 $= z(x \oplus y) + xy$

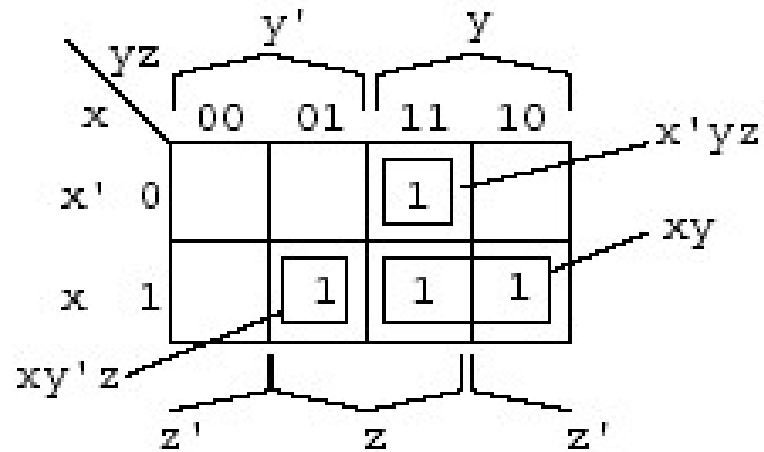$(x \oplus y)$ is already used for the sum S




Full Adder

Putting them together
we get:

$$S = x \oplus y \oplus z$$

$$C = z(x \oplus y) + xy$$

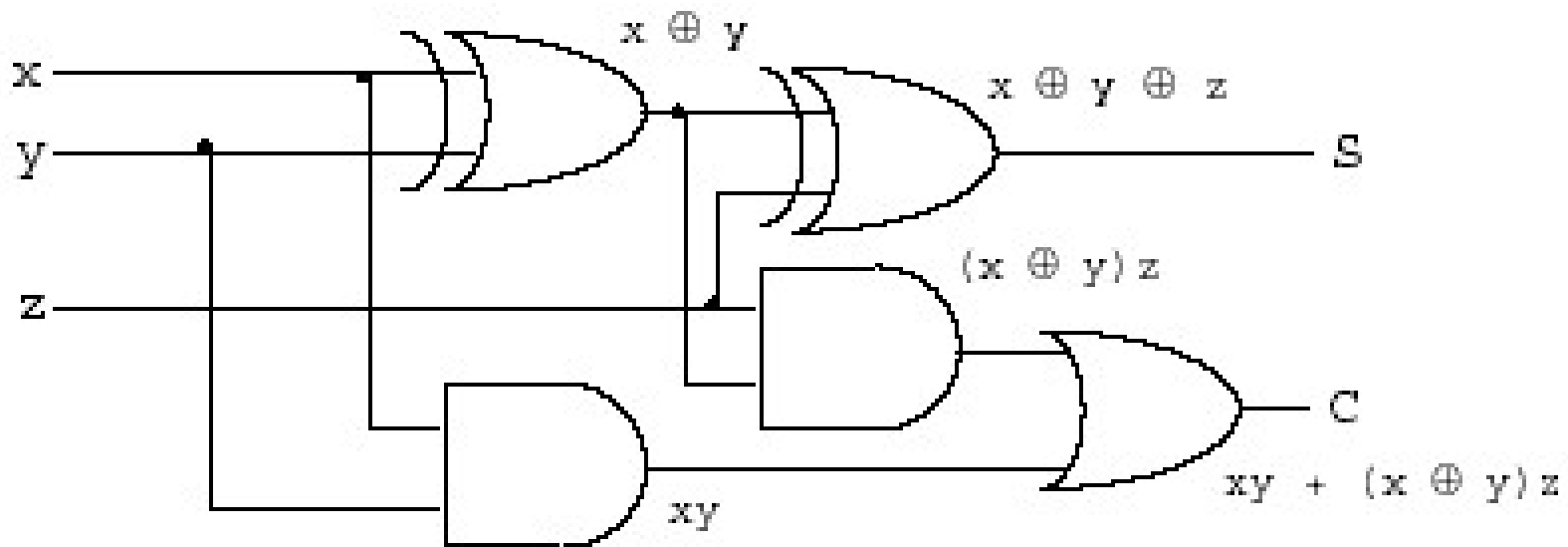

The logic diagram for the full adder